 
 


数字逻辑设计

高翠芸

School of Computer Science

gaocuiyun@hit.edu.cn

Our World
in Data

Transistor count

50,000,000,000

10,000,000,000

5,000,000,000

1,000,000,000

500,000,000

100,000,000

50,000,000

10,000,000

5,000,000

1,000,000

500,000


100,000

50,000

10,000

5,000


1,000

 

Data source: Wikipedia (wikipedia.org/wiki/Transistor_count)

OurWorldinData.org – Research and data to make progress against the world's largest problems.

 Licensed under CC-BY by the authors Hannah Ritchie and Max Roser.









英伟达3个月卖出800吨H100！云服务供应商的大规模H100集群容量即将耗尽，全球陷入GPU短缺——整体算来，全球公司需要约432000张H100。

by 新智元

Path to 100 Million Users (stylized)

  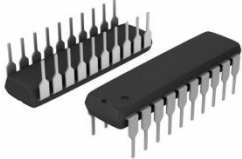

集成电路的分类

分类	单芯片内集成的逻辑门数量	集成内容	器件封装	需要掌握的内容
小规模 (SSI)	<10 gates	逻辑门、触发器等		① 学会查阅器件资料； ② 典型集成电路芯片的功能、外特性； ③ 能熟练运用并完成设计要求。
中规模 (MSI)	10~100 gates	译码器、计数器、加法器等模块		
大规模 (LSI)	100~10000 gates	存储器、微处理器或复杂的数字系统		① 了解典型PLD集成芯片的功能和特性； ② 能够使用HDL语言完成逻辑设计；
超大规模 (VLSI)	>10000 gates			

多级门电路

前提：忽略输入端原、反变量的差别。

门的级数——

电路输入与输出之间串联的门的最大数值

□ 二级电路

AND-OR 电路（积之和）


OR-AND 电路（和之积）

□ 三级电路

OR-AND-OR 电路

□ 各门没有特定的排列顺序

□ 输出门可以使与门也可以是或门

 


多级门电路

1. 二级电路

AND-OR 电路（积之和）

$$f = a'c'd + bc'd + bcd' + acd'$$


5个门, 16 个输入端

 

OR-AND 电路（和之积）

$$f = (c + d)(a' + b + c)(c' + d')(a + b + c')$$

5个门, 14 个输入端

 

ab					
cd		00	01	11	10
		0	0	0	0
00	0	0	0	0	0
01	1	1	1	0	0
11	0	0	0	0	0
10	0	1	1	1	0


多级门电路

1. 二级电路

AND-OR 电路（积之和）

$$f = a'c'd + bc'd + bcd' + acd'$$

5个门, 16 个输入端

 


2. 三级电路


OR-AND-OR 电路

$$f = c'd(a' + b) + cd'(a + b)$$

5个门, 12 个输入端

 


二级门电路的8种基本形式——1

 


二级门电路的8种基本形式——2



 
$$F = (A + B + C)(A + B' + C')(A + C' + D) \quad (7-18)$$


 
$$F = (A'B'C')' \cdot (A'BC)' \cdot (A'CD')' \quad (7-21)$$


   
$$F = [(A + B + C)' + (A + B' + C')' + (A + C' + D)']' \quad (7-19)$$




$$F = (A'B'C' + A'BC + A'CD')' \quad (7-20)$$

多级门电路设计实例

- 设计组合电路，对输入的2个二进制数 $X=X_1X_2$ 和 $Y=Y_1Y_2$ 比较，当 $X>Y$ ，输出 $F=1$ ；否则， $F=0$ 。

① 确定输入输出

 

② 真值表


X_1	X_2	Y_1	Y_2	F	X_1	X_2	Y_1	Y_2	F
0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	0	1	0	0
0	0	1	1	0	1	0	1	1	0
0	1	0	0	1	1	1	0	0	1
0	1	0	1	0	1	1	0	1	1
0	1	1	0	0	1	1	1	0	1
0	1	1	1	0	1	1	1	1	0

多级门电路

③ 最简二级与或电路

$$F = X_1 \bar{Y}_1 + X_2 \bar{Y}_1 \bar{Y}_2 + X_1 X_2 \bar{Y}_2$$

$Y_1 Y_2$ $X_1 X_2$		$Y_1 Y_2$			
		00	01	11	10
00	0	0	0	0	0
01	1	0	0	0	0
11	1	1	0	1	0
10	1	1	0	0	1


 


多级门电路

④ 采用单一逻辑门(与非门)设计

$$F = X_1 \bar{Y}_1 + X_2 \bar{Y}_1 \bar{Y}_2 + X_1 X_2 \bar{Y}_2$$
  
$$= \overline{(\overline{X_1 \bar{Y}_1}) (\overline{X_2 \bar{Y}_1 \bar{Y}_2}) (\overline{X_1 X_2 \bar{Y}_2})}$$



二级门电路的设计

任何逻辑都可以用二级门电路实现


$$F(X,Y,Z) = \sum_{XYZ} (1,6,7) = \prod_{XYZ} (0,2,3,4,5)$$

$$F'(X,Y,Z) = \sum_{XYZ} (0,2,3,4,5) = \prod_{XYZ} (1,6,7)$$


NAND and **NOR** gates:

相比与门、或门——速度更快；价格便宜；使用的器件更少

CMOS NAND gate

 


CMOS AND gate

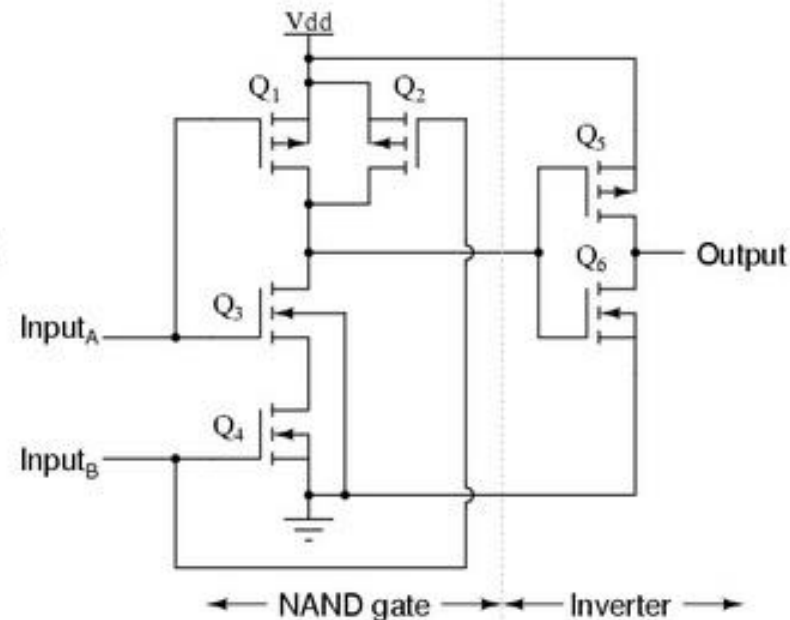


与非门/或非门节省空间和门延迟。

CMOS NOR gate

 

CMOS OR gate

 


加减法器和OC门

- 半加器
- 全加器
- 多位加法器
- 全减器
- OC门

半加器 (Half Adder)

功能：对两个1位二进制数执行相加运算

 


$$S_i = a_i \oplus b_i$$

$$C_{i+1} = a_i b_i$$


真值表

a_i	b_i	S_i	C_{i+1}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

利用单一逻辑门与非门实现半加器
 
$$\left\{ \begin{aligned} S_i &= \bar{a}_i b_i + a_i \bar{b}_i = \bar{a}_i b_i + a_i \bar{b}_i + a_i \bar{a}_i + b_i \bar{b}_i \\ &= a_i (\bar{a}_i + \bar{b}_i) + b_i (\bar{a}_i + \bar{b}_i) = a_i \overline{a_i b_i} + b_i \overline{a_i b_i} \\ &= \overline{a_i a_i b_i} \overline{b_i a_i b_i} \\ C_{i+1} &= \overline{\overline{a_i b_i}} \end{aligned} \right.$$




全加器 (Full Adder)

$$\begin{array}{r} 1\ 0\ 1\ 1\ \dots\dots\dots A \\ 1\ 1\ 1\ 0\ \dots\dots\dots B \\ + \qquad\qquad 0\ \dots\dots\dots C_i \\ \hline \qquad\qquad\qquad \dots\dots\dots S_i \end{array}$$

$$A = a_3 a_2 a_1 a_0 = 1011$$

$$B = b_3 b_2 b_1 b_0 = 1110$$

全加器表示

 

a_i	b_i	C_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

S_i

		$b_i c_{i-1}$			
		00	01	11	10
a_i	0	0	1	0	1
	1	1	0	1	0

C_{i+1}

		$b_i c_i$			
		00	01	11	10
a_i	0	0	0	1	0
	1	0	1	1	1



$$\begin{aligned}
 S_i &= \bar{a}_i \bar{b}_i c_i + a_i \bar{b}_i \bar{c}_i + a_i \bar{b}_i c_i + a_i b_i \bar{c}_i \\
 &= (\bar{a}_i \bar{b}_i + a_i b_i) c_i + (a_i \bar{b}_i + a_i \bar{b}_i) \bar{c}_i \\
 &= (\overline{a_i \oplus b_i}) c_i + (a_i \oplus b_i) \bar{c}_i \\
 &= a_i \oplus b_i \oplus C_i
 \end{aligned}$$

$$C_{i+1} = (a_i \oplus b_i) C_i + a_i b_i$$

全加器逻辑表示



◆ solution 1:
  
$$\begin{cases} S_i = a_i \oplus b_i \oplus C_i \\ C_{i+1} = (a_i \oplus b_i) C_i + a_i b_i \end{cases}$$



全加器逻辑表示 (2)

◆ solution 2

  

$$S_i = a_i \oplus b_i \oplus C_i$$

$$C_{i+1} = (a_i \oplus b_i) C_i + a_i b_i$$



$$\begin{cases} S_i = a_i \oplus b_i \\ C_{i+1} = a_i b_i \end{cases}$$


全加器的应用

典型芯片

- 74LS82: 2-bit adder
- 74LS283: 4-bit adder

二进制数 $A_3 A_2 A_1 A_0$	余三码 $S_3 S_2 S_1 S_0$	二进制数 $A_3 A_2 A_1 A_0$	余三码 $S_3 S_2 S_1 S_0$
0 0 0 0	0 0 1 1	1 0 0 0	1 0 1 1
0 0 0 1	0 1 0 0	1 0 0 1	1 1 0 0
0 0 1 0	0 1 0 1	1 0 1 0	×
0 0 1 1	0 1 1 0	1 0 1 1	×
0 1 0 0	0 1 1 1	1 1 0 0	×
0 1 0 1	1 0 0 0	1 1 0 1	×
0 1 1 0	1 0 0 1	1 1 1 0	×
0 1 1 1	1 0 1 0	1 1 1 1	×

应用——余3码产生器

 


$A_3 A_2 A_1 A_0$: 输入 8421 BCD码

$S_3 S_2 S_1 S_0$: 输出余3码

$$S = A + 0011$$

4位并行加法器

(1) 串行进位

 

$$A = A_3A_2A_1A_0 = 1011$$

$$B = B_3B_2B_1B_0 = 1110$$

$$S_i = a_i \oplus b_i \oplus C_i$$

$$C_{i+1} = (a_i \oplus b_i) C_i + a_i b_i$$

- 优点：线路简单
- 缺点：串行进位，运算速度慢
- 关键：进位形成时间
- 解决方案：改串行进位为并行进位

4位并行加法器

P83

(2) 超前进位


$$C_{i+1} = (A_i \oplus B_i) C_i + A_i B_i$$

$$A = A_3 A_2 A_1 A_0 = 1011$$

$$B = B_3 B_2 B_1 B_0 = 1110$$

$$C_{i+1} = P_i C_i + G_i$$

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

——进位迭代公式

$$C_1 = P_0 C_0 + G_0$$


$$C_2 = P_1 C_1 + G_1 = P_1 P_0 C_0 + P_1 G_0 + G_1$$

$$C_3 = P_2 C_2 + G_2 = P_2 P_1 P_0 C_0 + P_2 P_1 G_0 + P_2 G_1 + G_2$$


$$C_4 = P_3 C_3 + G_3 = P_3 P_2 P_1 P_0 C_0 + P_3 P_2 P_1 G_0 + P_3 P_2 G_1 + P_3 G_2 + G_3$$

4位并行加法器

(2) 超前进位

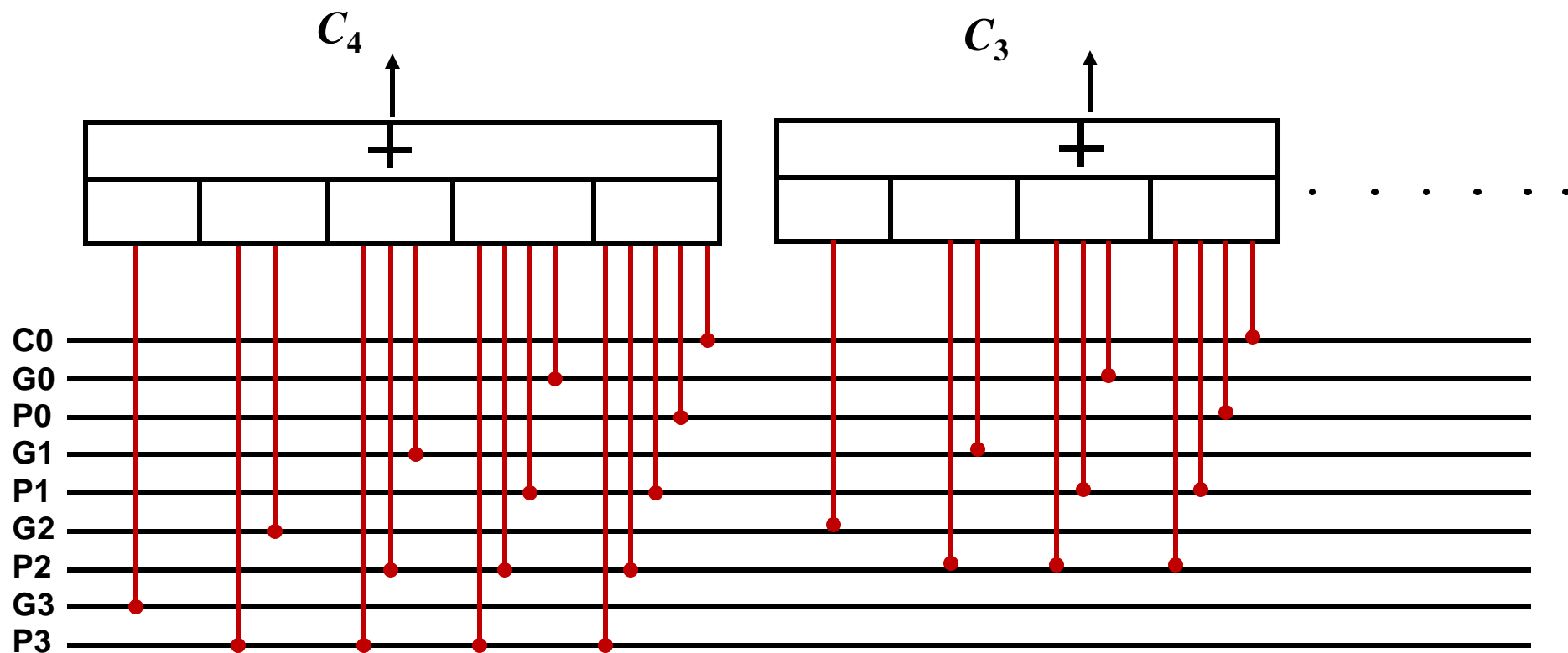

4位并行加法器

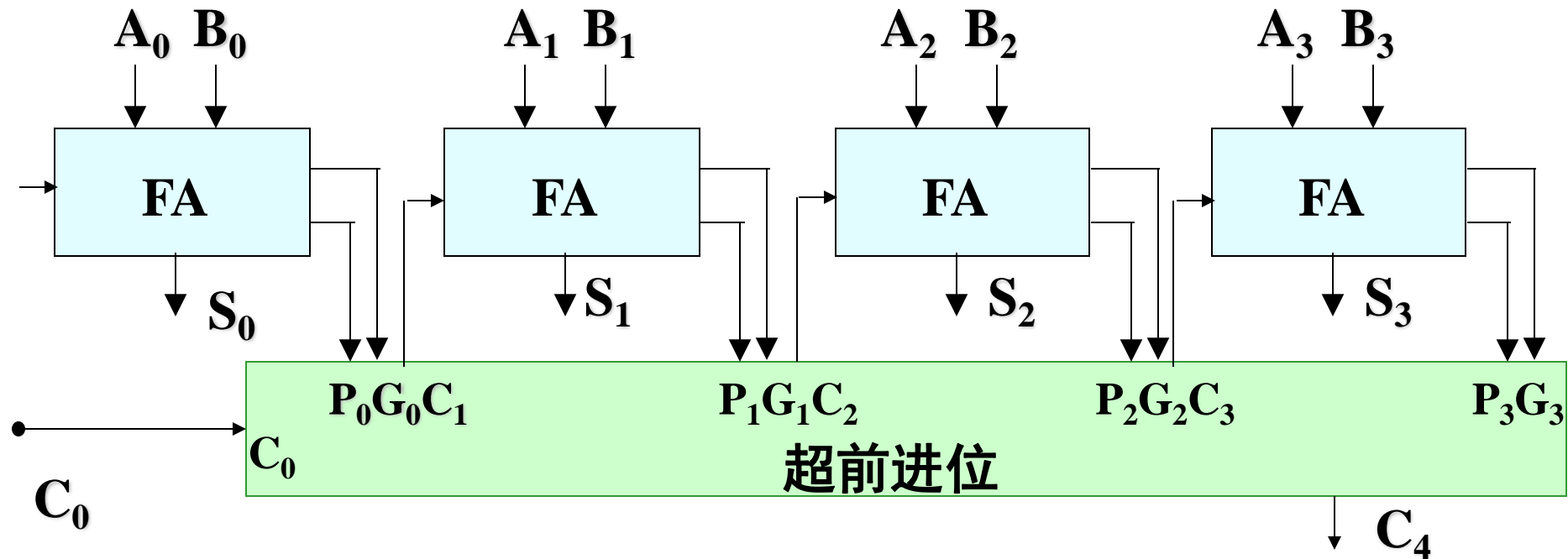

$$P_i = A_i \oplus B_i \quad G_i = A_i B_i$$

$$C_1 = P_0 C_0 + G_0$$


$$C_2 = P_1 C_1 + G_1 = P_1 P_0 C_0 + P_1 G_0 + G_1$$

$$C_3 = P_2 C_2 + G_2 = P_2 P_1 P_0 C_0 + P_2 P_1 G_0 + P_2 G_1 + G_2$$

$$C_4 = P_3 C_3 + G_3 = P_3 P_2 P_1 P_0 C_0 + P_3 P_2 P_1 G_0 + P_3 P_2 G_1 + P_3 G_2 + G_3$$

全减器 (Binary Full Subtractor)
 
$$\begin{array}{r}
 1\ 1\ 1\ 0 \dots\dots\dots A \\
 1\ 0\ 1\ 1 \dots\dots\dots B \\
 -\ 0 \quad \quad \quad 0 \dots\dots\dots C_i \\
 \hline
 \dots\dots\dots D_i
 \end{array}$$



$$A = a_3 a_2 a_1 a_0 = 1110$$

$$B = b_3 b_2 b_1 b_0 = 1011$$

真值表

a_i	b_i	C_i	D_i	C_{i+1}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

全减器——例


真值表

a_i	b_i	C_i	D_i	C_{i+1}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\begin{cases} D_i = a_i \oplus b_i \oplus C_i \\ C_{i+1} = (C_i \oplus b_i) \bar{a}_i + C_i b_i \end{cases}$$


	$b_i c_i$	00	01	11	10
a_i	0	0	1	0	1
	1	1	0	1	0

	$b_i c_i$	00	01	11	10
a_i	0	0	1	1	1
	1	0	0	1	0

 

OC门（集电极开路门：Open Collector Gate）

$$F = \overline{AB}$$

 


- 几个OC门的输出端可以直接互连：“线与”
- 使用时必须加负载/上拉电阻

OC门&线与

$$F = F_1 \cdot F_2 = \overline{A_1 B_1 C_1} \cdot \overline{A_2 B_2 C_2}$$

不使用OC门，
需要2个与非门、1个与门

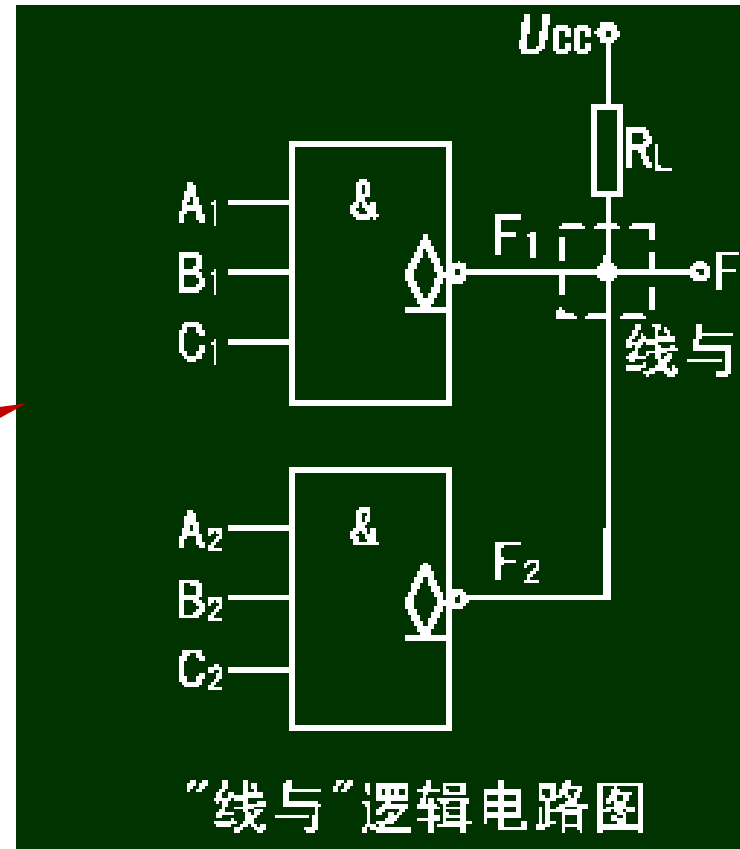

小 结

- 半加器
- 全加器
- 多位加法器
- 全减器
- 0C门